

SQUISHY CIRCUITS

**BROUGHT TO YOU BY THE RUBBER BAND
PROJECT**

HOW DO ARTISTS AND DESIGNERS USE LIGHTS AND CIRCUITRY IN THEIR WORK?




FASHION AND TEXTILES






WHAT IS A CIRCUIT ?



TURN TO A PARTNER AND DEFINE

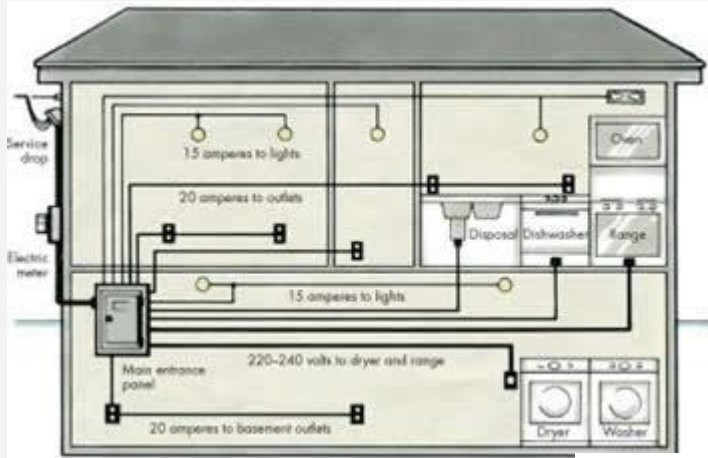

Closed circuit




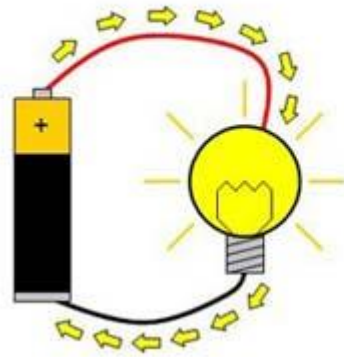


Open circuit

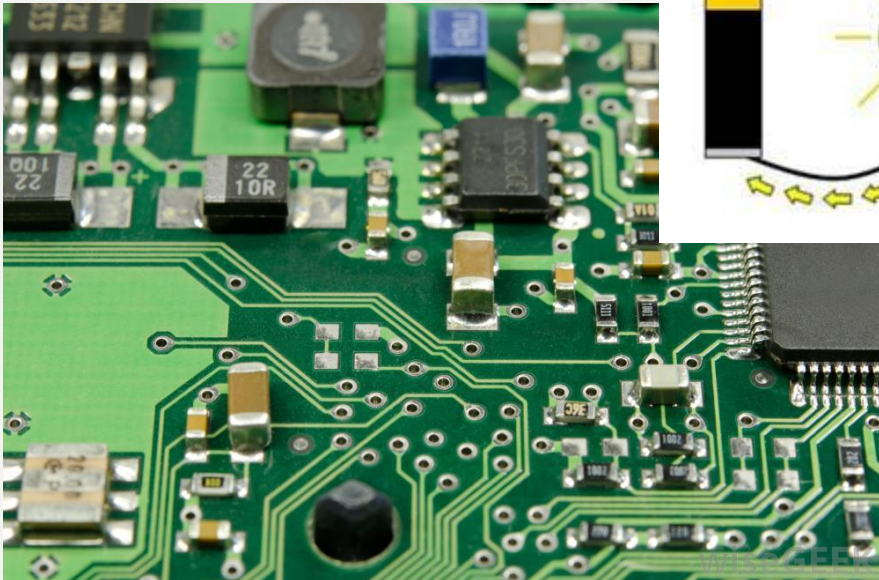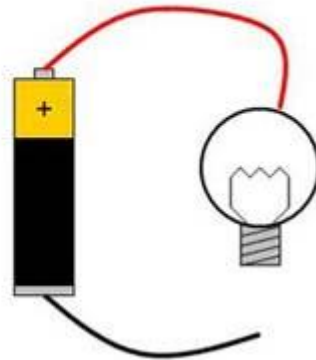


A CIRCUIT IS “A ROUGHLY CIRCULAR LINE, ROUTE, OR MOVEMENT THAT STARTS AND FINISHES AT THE SAME PLACE.”

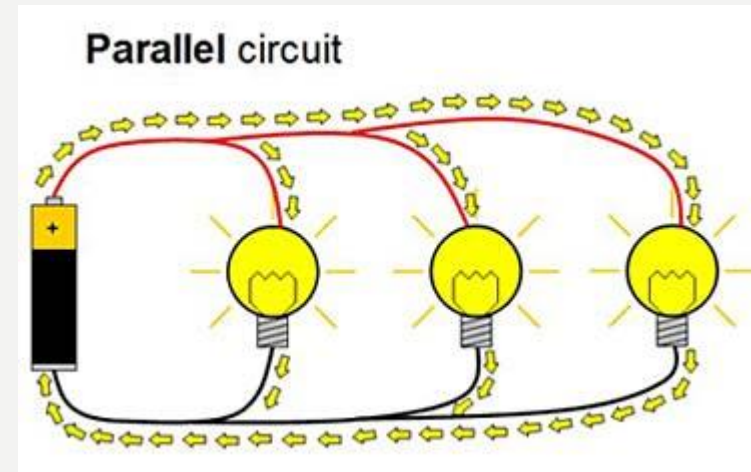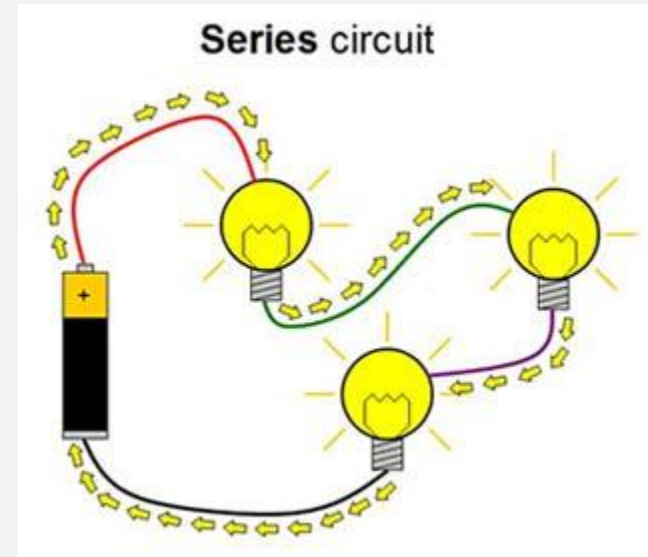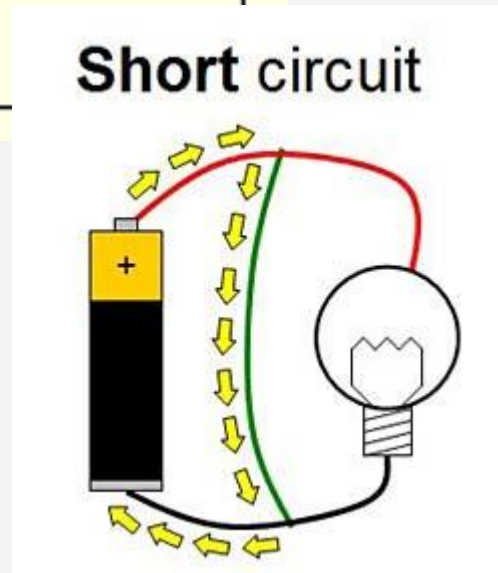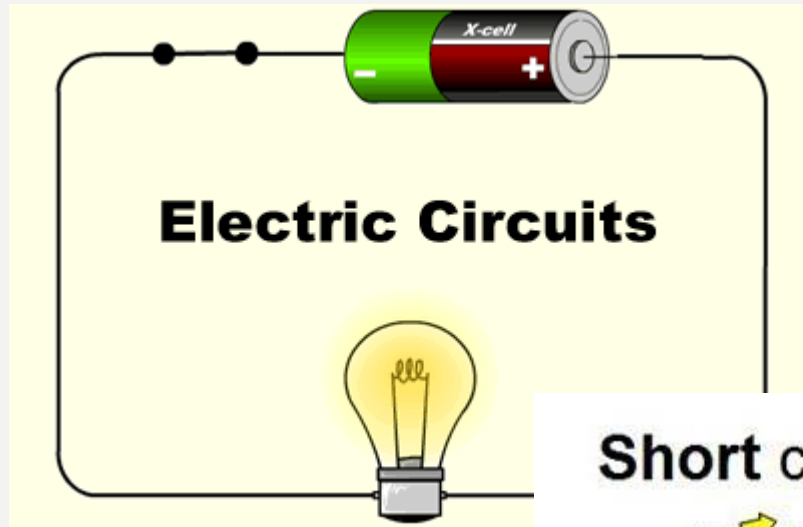
NOW LET'S PLAY! CAN YOU MAKE THESE CIRCUITS?



SQUISHY CIRCUITS FROM OUR STUDENTS

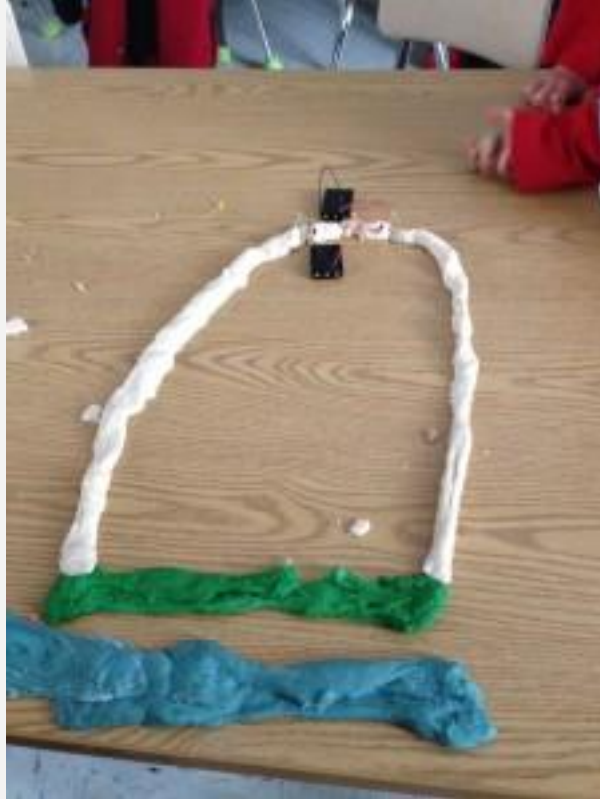

WHAT CAN YOU MAKE?

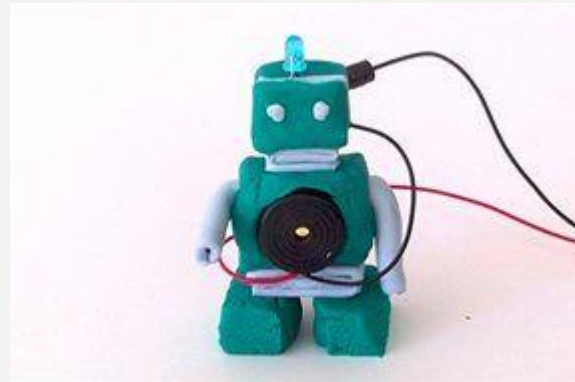



THANK YOU!

WWW.RUBBERBANDPROJECT.ORG

STEVE GROSS

STEVE@RUBBERBANDPROJECT.ORG